

$$V_{in}(t) = i(t)R + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt$$

$$V_{in}(s) = R \cdot s I(s) + L \cdot s^2 I(s) + \frac{1}{C} I(s)$$


$$V_{in}(s) = \left(L s^2 + \frac{1}{C} + R s \right) \cdot I(s)$$

$$\frac{I(s)}{V_{in}(s)} = \frac{1}{L s^2 + R s + \frac{1}{C}}$$

$$V_c(s) = \frac{1}{C} I(s)$$

$$\boxed{I(s) = C V_c(s)} ; V_c = V_{out}$$
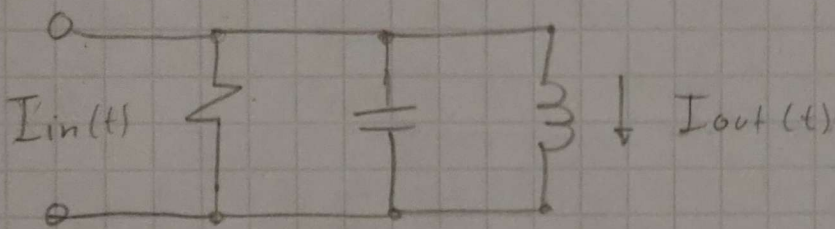
$$12/ \frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{CLs^2 + CRs + 1}$$



$$I_{in}(t) = \frac{V(t)}{R} + C \frac{dV(t)}{dt} + I_{out}(t)$$

$$V_L(t) = L \frac{di_L(t)}{dt} ; \quad i_L = I_{out}$$

Y, que el voltaje es el mismo, reemplazamos:

$$I_{in}(t) = \frac{1}{R} \left(L \frac{di_L(t)}{dt} \right) + C \frac{d}{dt} \left(\frac{di_L(t)}{dt} \right) + I_{out}$$

$$I_{in}(s) = \frac{L}{R} \cdot s I_L(s) + LC s^2 I_L(s) + I_L(s)$$

Organizando nos queda:

R/

$$\frac{I_L(s)}{I_{in}(s)} = \frac{1}{LC s^2 + \frac{L}{R} s + 1}$$