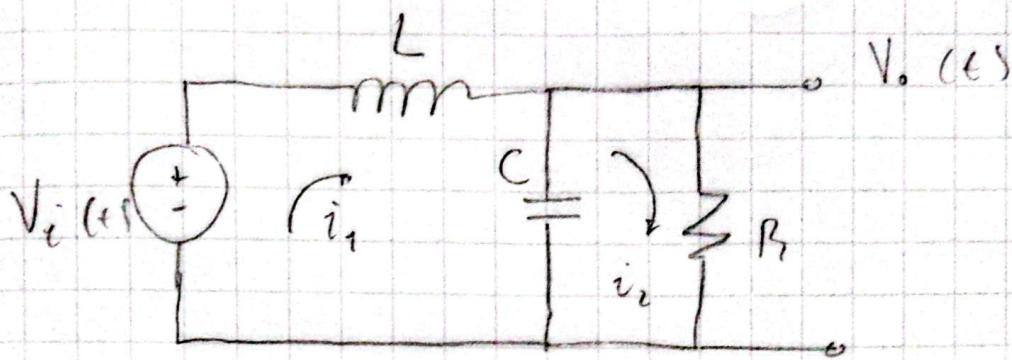




Malla 1:

$$V_i(t) = L \frac{di_1(t)}{dt} + \frac{1}{C} \int i_1(t) - i_2(t) dt$$

Aplicando Laplace:

$$V_i(s) = L s I_1(s) + \frac{1}{C s} (I_1(s) - I_2(s))$$

Malla 2:

$$0 = \frac{1}{C} \int i_2(t) - i_1(t) dt + R \cdot i_2(t)$$

Aplicando Laplace:

$$V_{i2}(t) = \frac{1}{C s} (I_2(s) - I_1(s)) + R I_2(s)$$

Despejamos $I_1(t)$:

$$I_1(s) = (1 + RSC) I_2(s)$$

Reemplazamos en la entrada:

$$V_i(s) = LS(1 + RSC) I_2(s) + \frac{1}{CS} \left((1 + CRs) I_2(s) - I_2(s) \right)$$

$$V_i(s) = LS I_2(s) + CLS^2 R I_2(s) + \frac{I_2(s)}{CS} + R I_2(s) - \frac{I_2(s)}{CS}$$

$$V_i(s) = LS I_2(s) + CLS^2 R I_2(s) + R I_2(s)$$

$$V_i(s) = I_2(s) (LS + CLR s^2 + R)$$

Sabemos que: $V_o(s) = R \cdot I_2(s)$

Entonces:

$$V_i(s) = \frac{V_o(s)}{R} \cdot (CLR s^2 + LS + R)$$

Lo llevamos a la forma: $H(s) = \frac{\text{salida}}{\text{entrada}}$

$$\frac{V_o(s)}{V_i(s)} = \frac{R}{CLR s^2 + LS + R}$$

Quedamos la resistencia del numerador:

$$\frac{V_o(s)}{V_i(s)} = \frac{(R) \cdot \frac{1}{R}}{(CLR s^2 + Ls + R) \cdot \frac{1}{R}}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{L}{CLs^2 + \frac{Ls}{R} + 1}$$

Así, nuestra función de transferencia queda:

$$\cancel{V} H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{CLs^2 + \frac{Ls}{R} + 1}$$